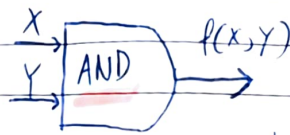


Digital Fundamentals - Logic Gates


Boolean Functions

X AND Y

X	Y	f
0	0	0
0	1	0
1	0	0
1	1	1



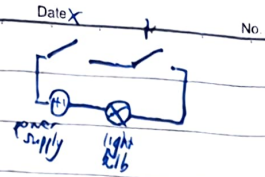
$$f(x,y) = \begin{cases} 1 & \text{when } x=1 \text{ \& } y=1 \\ 0 & \text{otherwise} \end{cases}$$



X OR Y


X	Y	OR
0	0	0
0	1	1
1	0	1
1	1	1

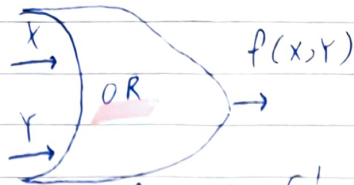

$$f(x,y) = \begin{cases} 1 & \text{when } x=1 \text{ OR } y=1 \\ 0 & \text{otherwise} \end{cases}$$




X	Not	Inverts
0	1	
1	0	

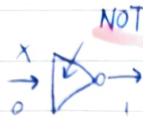


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Inverts AND Gate

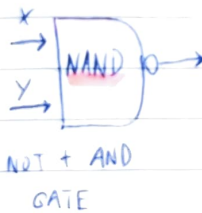

NOT + AND GATE

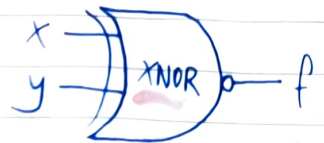


X	Y	f
0	0	1
0	1	0
1	0	0
1	1	1

[2 1s or 0s]

X	Xor	Y
0	0	0
0	1	1
1	0	1
1	1	0

1 if different inputs

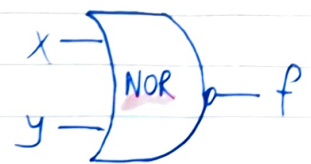

X	Y	f
0	0	1
0	1	0
1	0	0
1	1	0